

VLSI SYSTEM DESIGN LAB(ECE3001)

(BY PROF.JAGANNADHA NAIDU K)

TASK-2

CMOS INVETRER AND 2INPUT NOR GATE ANALYSIS



SLOT-L23+L24



NAME:SIDDHANT AGARWAL

REGISTER NO:-17BEC0431


TASK-2A

AIM: TO measure the voltage transfer characteristics of CMOS inverter and measure the time delay and average power dissipation.

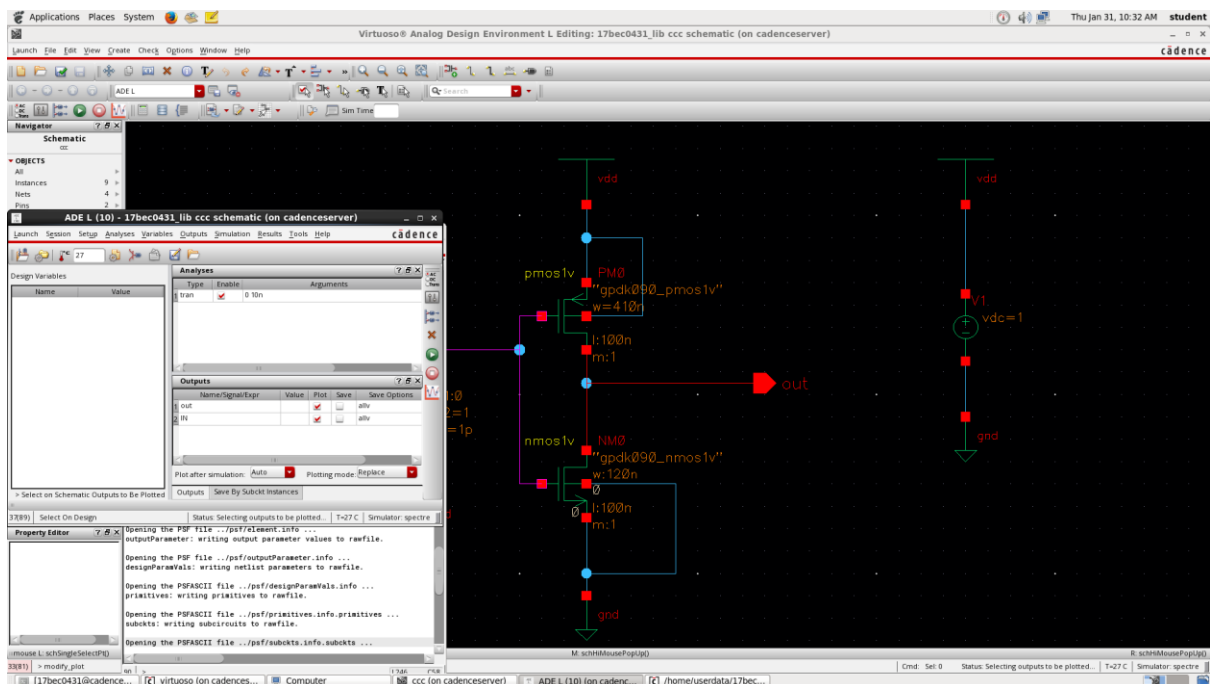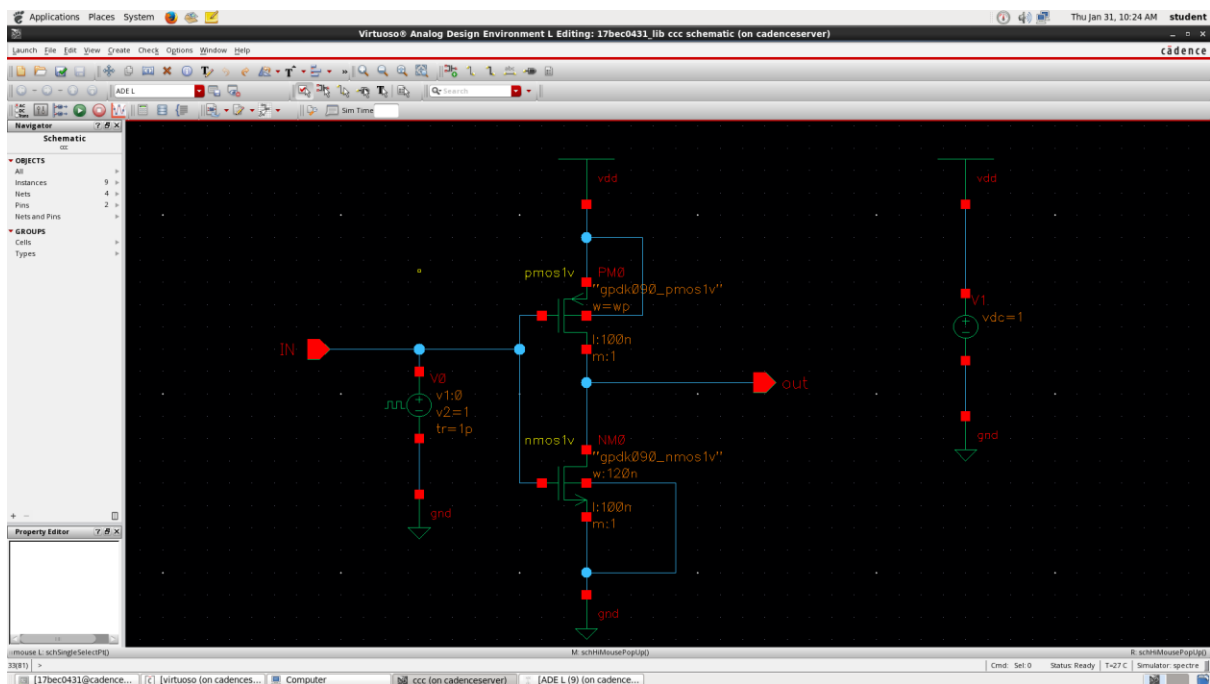
CIRCUIT DIAGRAM

  
PLOTS:DC TRANSFER CHARACTERISTICSPARAMETRIC ANALYSIS FOR W_p 

TIME DELAY

 

 POWER CLACULATION GRAPH USING .PWR SIGNAL



 

FOLLOWING ARE THE OBSERVATIONS TAKEN FROM ABOVE GRAPHS

(Rising falling delay) $T_{pdf} = 7.483\text{ps}$

(Falling rising delay) $T_{pdf} = 3.91\text{ps}$

Propagation delay $= (T_{pdf} + T_{pdf}) / 2 = 5.69\text{ps}$

Average power dissipation $= 636.5 \times 10^{-9}$

INFERENCE

We GET $V_{IN}=V_{DD}/2=V_{OUT}$

At $B_n=B_p$

RESULT

(Rising falling delay) $T_{pdrf}=7.483ps$

(Falling rising delay) $T_{pdfr}=3.91ps$

Propagation delay= $(T_{pdrf}+T_{pdfr})/2 =5.69ps$


Average power dissipation= 636.5×10^{-9}

TASK2-B


AIM :To examine the transient characteristic of CMOS 2 input NOR gate and also to calculate the delay and average power.



CIRCUIT DIAGRAM



When both A and B are varying(tphl)


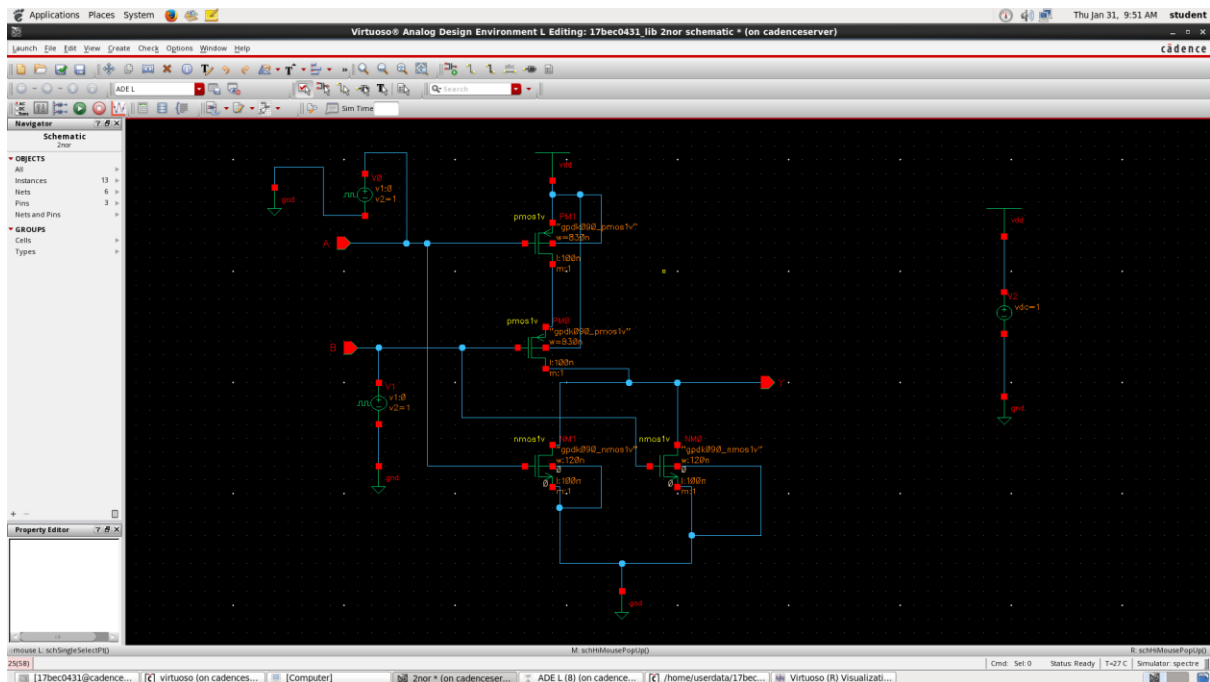



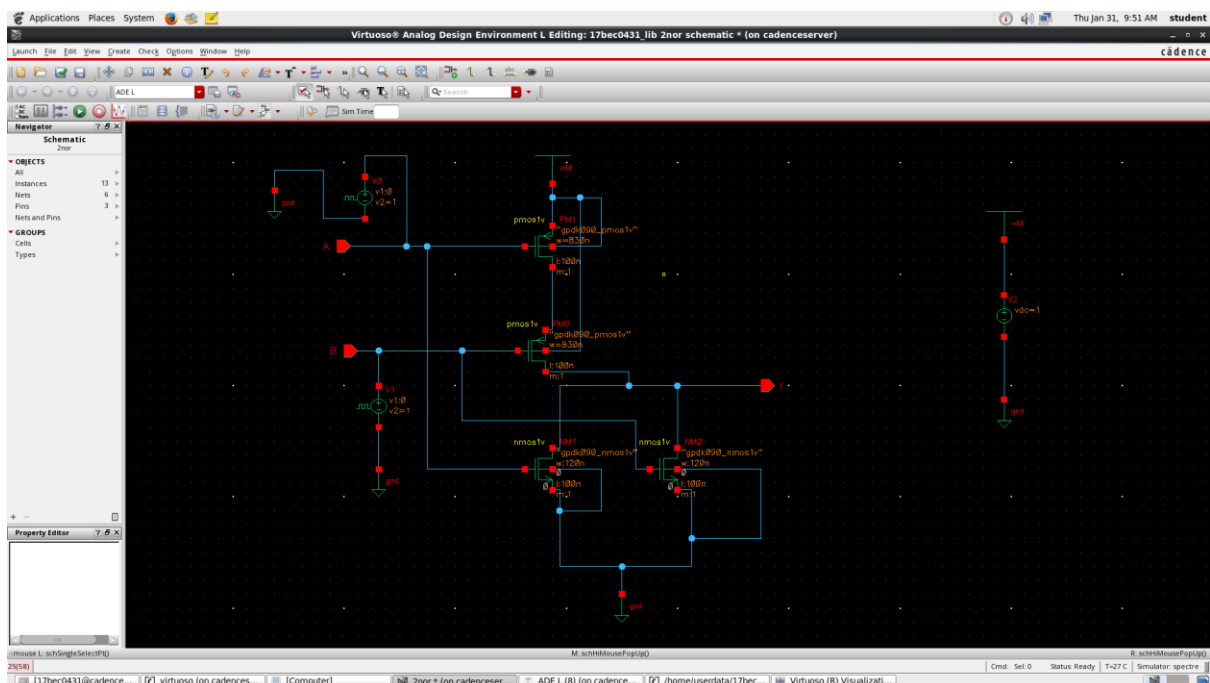
When only A is varying and B is set to 0V dc(tphl)





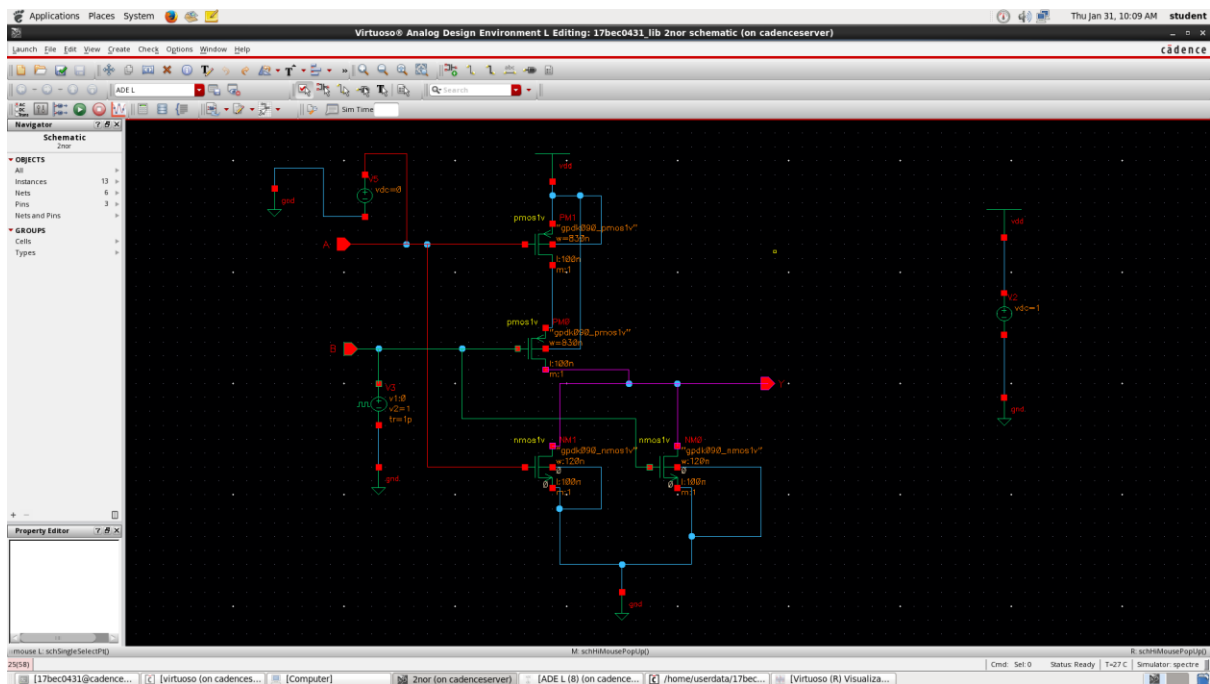
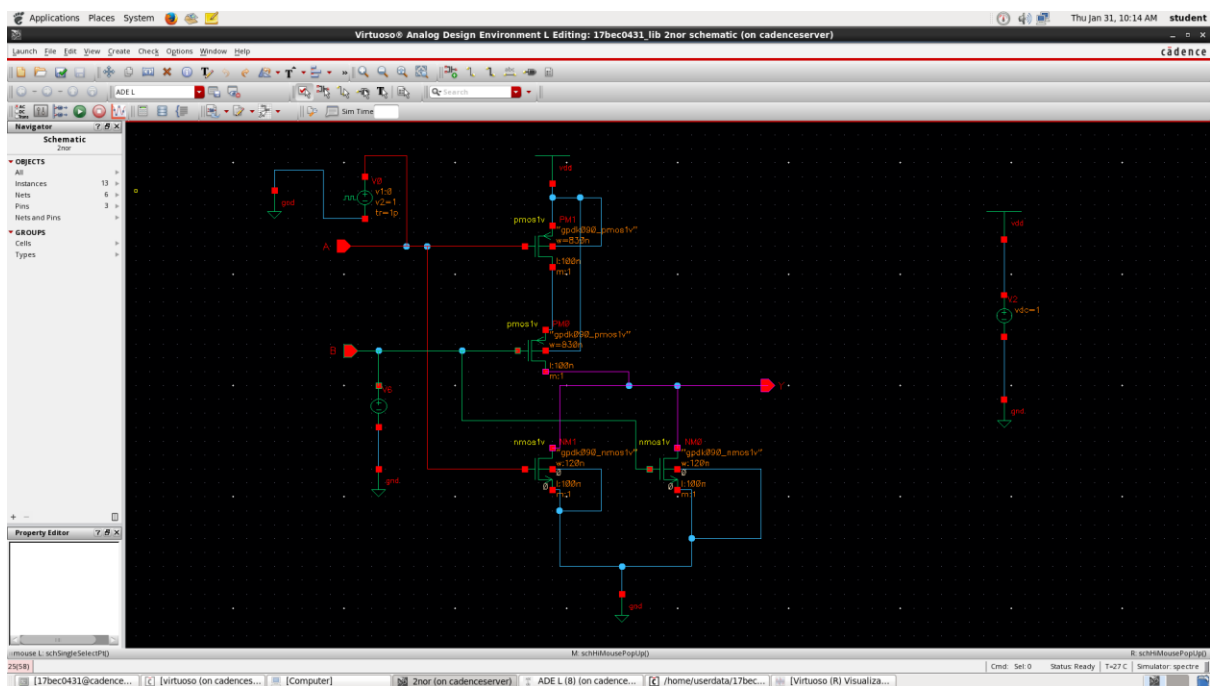
When A is set to 0V dc and B is varying(tplh)When A is varying and B is set to 0V(tplh)

  
PLOTSFUNCTIONALITY(WHERE A AND B ARE INPUTS AND Y IS OUTPUT)CASE1: (00 TO 11)(T_{phl})

  Case1 with .pwr signalCase2 (00->10)(T_{phi})

 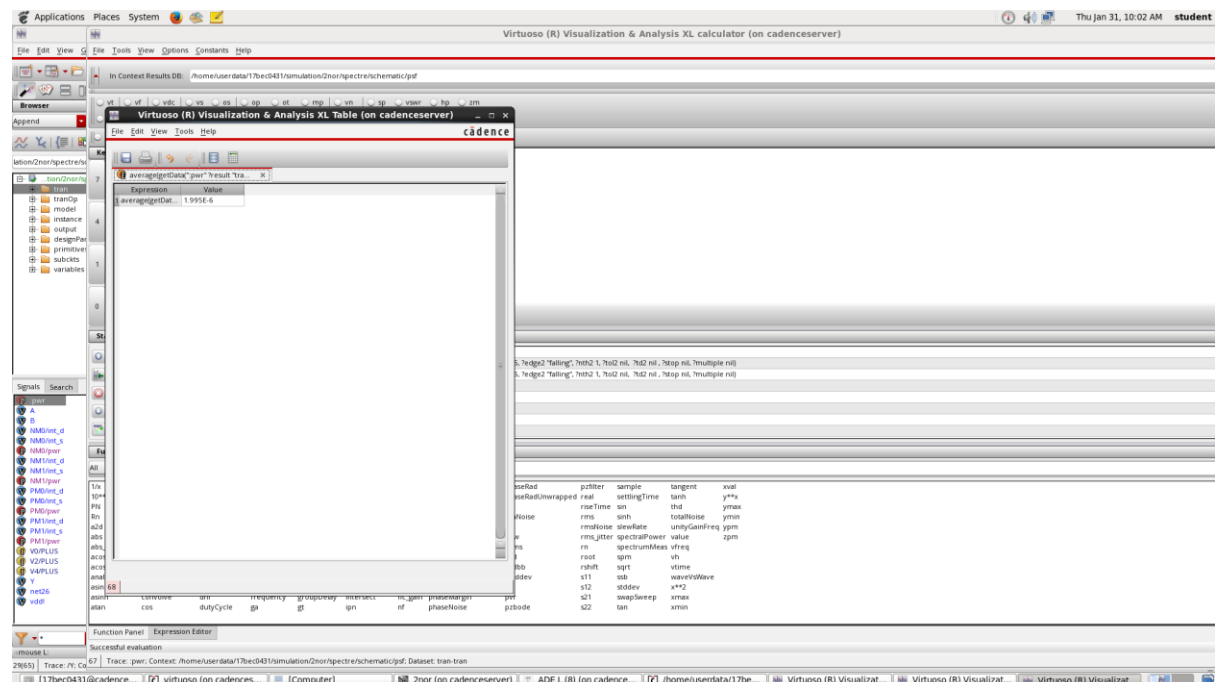Case2:with .pwr signalCase2:calculated average power

 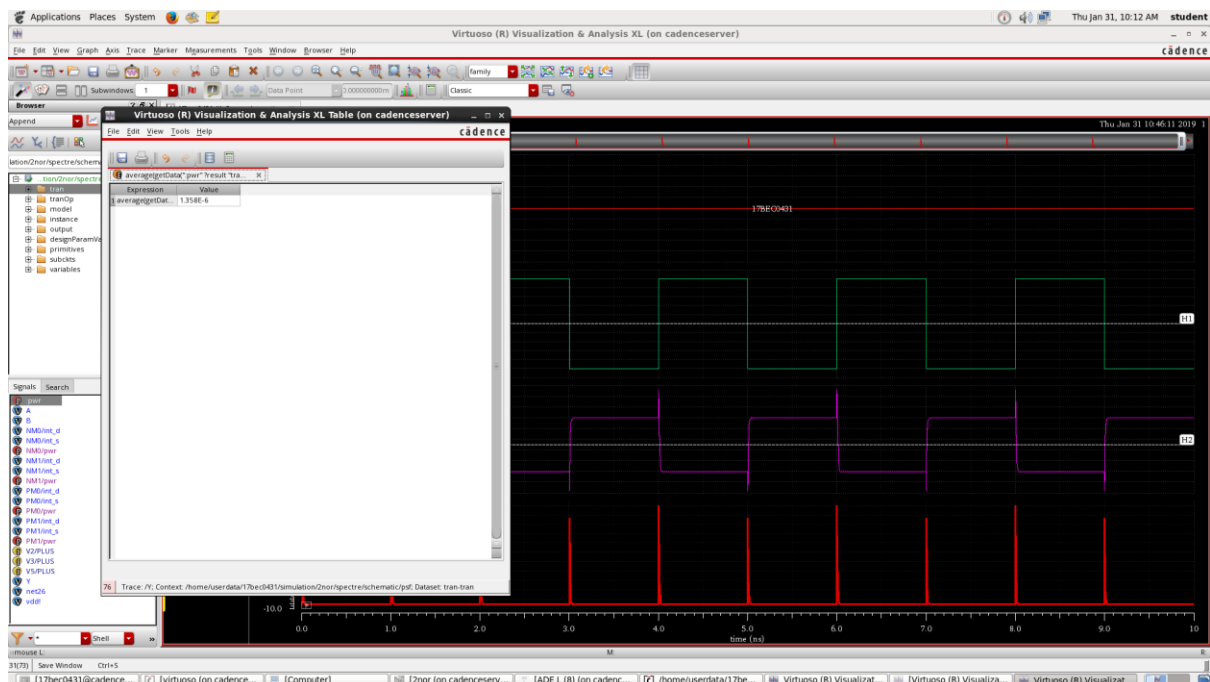Case3 (10->00)(T_{plh})**Case3:with .pwr and average power**

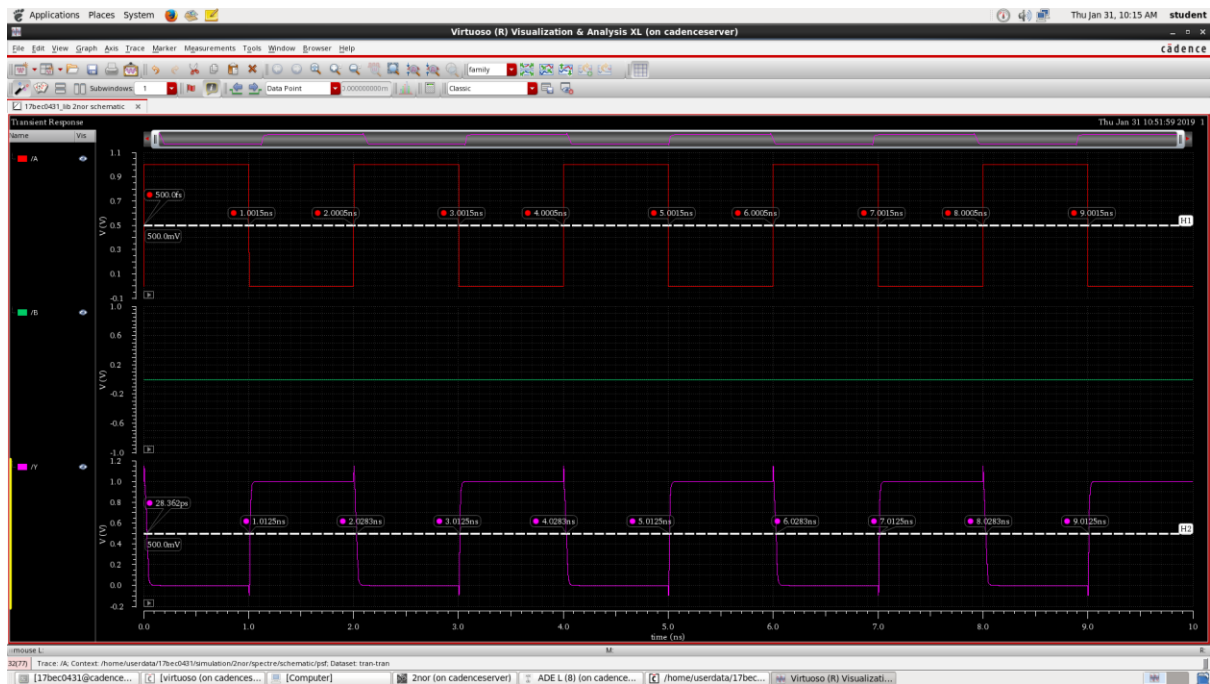 Case4: (10->00)(T_{plh})**Case4:with .pwr signal**

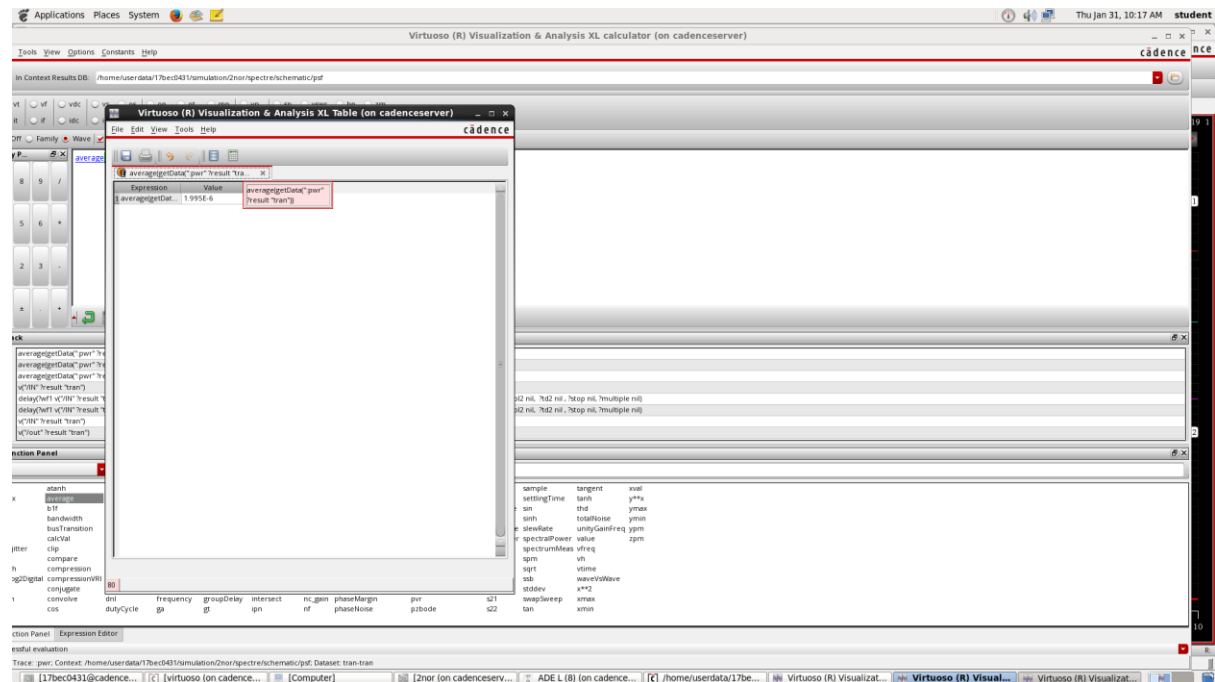Case4: calculated average power**OBSERVATION**

INPUT COMBINATIONS	SIGNAL MODE	TIME DELAY	AVERAGE POWER
00->11(A->Y)	Tp->high to low	9.4ps	2.18×10^{-6}
00->10(A->Y)	Tp->high to low	23.3ps	1.995×10^{-6}
01->00(B->Y)	Tp->low to high	7.6ps	1.35×10^{-6}
10->00(A->Y)	Tp->low to high	11ps	1.995×10^{-6}

INFERENCE:

When both the inputs are varying ,the average power is higher than other inputs.

Result:

Case1:time delay	9.4ps	average power	2.18×10^{-6}
Case2: time delay	23.3ps	average power	1.995×10^{-6}
Case3: time delay	7.6ps	average power	1.35×10^{-6}

Case4: time delay 11ps average power 1.995×10^{-6}